



# Welcome to The Logic Design Lab!

Fall 2020

## Lab 5: Keyboard and Audio Modules

Prof. Chun-Yi Lee

Department of Computer Science  
National Tsing Hua University

# Agenda

- Lab 5 Outline
- Lab 5 Basic Questions
- Lab 5 Advanced Questions



# Lab 5 Outline

- Basic questions (1%)
  - Individual assignment
  - Due on **11/19/2020**. Demonstration on your FPGA board (**In class**)
  - Only demonstration is necessary. Nothing to submit.
- Advanced questions (6%)
  - Group assignment
  - ILMS submission due on **11/26/2020. 23:59:59**.
    - **Submit your FPGA codes to ILMS by 11/26/2020. 15:00:00.**
  - Demonstration on your FPGA board (**In class**)
  - Assignment submission (**Submit to ILMS**)
    - Source codes and testbenches
    - Lab report in PDF

# Lab 5 Rules

- Please note that grading will be based on NCVerilog
- You can use **ANY** modeling techniques
- If not specifically mentioned, we assume the following SPEC
  - **CLK** is **positive edge triggered**
  - Synchronously reset the Flip-Flops when **RESET == 1'b0**

# Lab 5 Submission Requirements

- Source codes and testbenches
  - Please follow the templates **EXACTLY**
  - We will test your codes by TAs' testbenches
- Lab 5 report
  - Please submit your report in a single **PDF** file
  - Please **draw** the **block diagrams** and **state transition diagrams** of your designs
  - Please **explain** your designs in detail
  - Please **list** the contributions of each team member clearly
  - **Please explain how you test your design**
  - What you have **learned** from Lab 5

# Agenda

- Lab 5 Outline
- **Lab 5 Basic Questions**
- Lab 5 Advanced Questions



# Basic Questions

- Individual assignment
- FPGA demonstration (due on 11/19/2020. In class.)
  - Keyboard sample code
  - Audio sample code 1 & 2

# Basic FPGA Demonstration 1

- **Keyboard sample code**

- Please implement the keyboard sample codes released on ILMS


- **Audio sample codes**

- Please implement the audio sample codes 1 & 2 released on ILMS


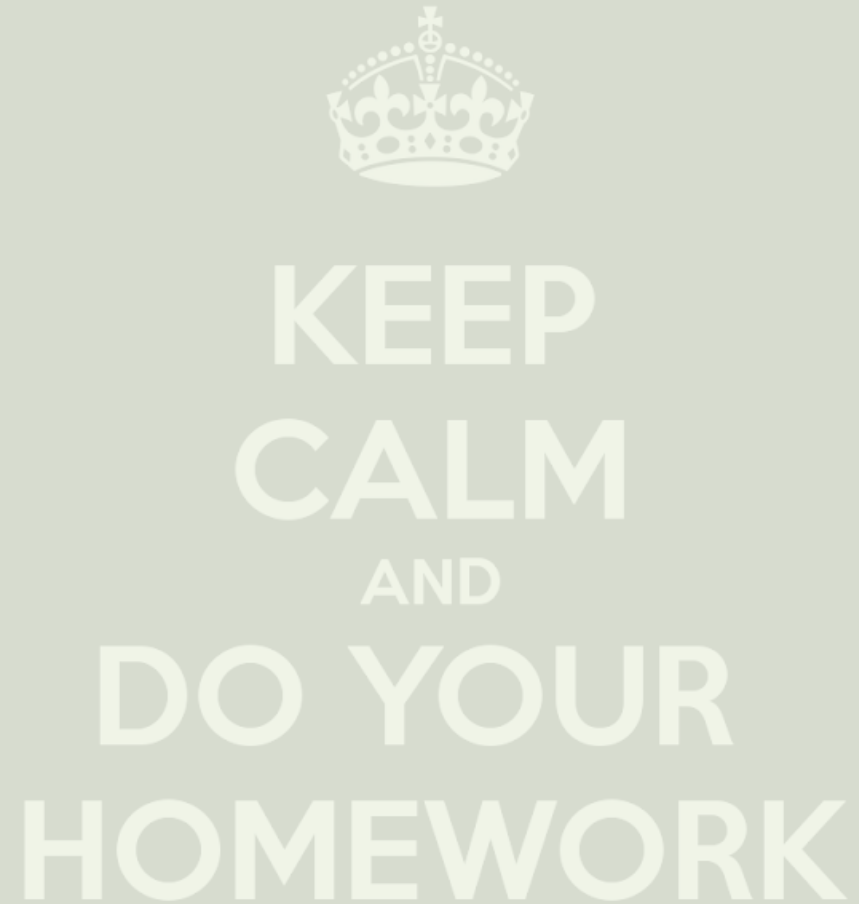
# Agenda

- Lab 5 Outline
- Lab 5 Basic Questions
- **Lab 5 Advanced Questions**




# Advanced Questions

- Group assignment
- Verilog questions
  - Source codes and the report due on 11/26/2020. 23:59:59.
  - Sliding window sequence detector
  - Traffic light controller
- FPGA demonstration (due on 11/26/2020. In class.)
  - Mixed keyboard and audio modules together
  - Vending machine
  - Please submit your source codes by 11/26/2020. 15:00:00.
  - We will only grade your demonstration based on your codes downloaded from ILMS.

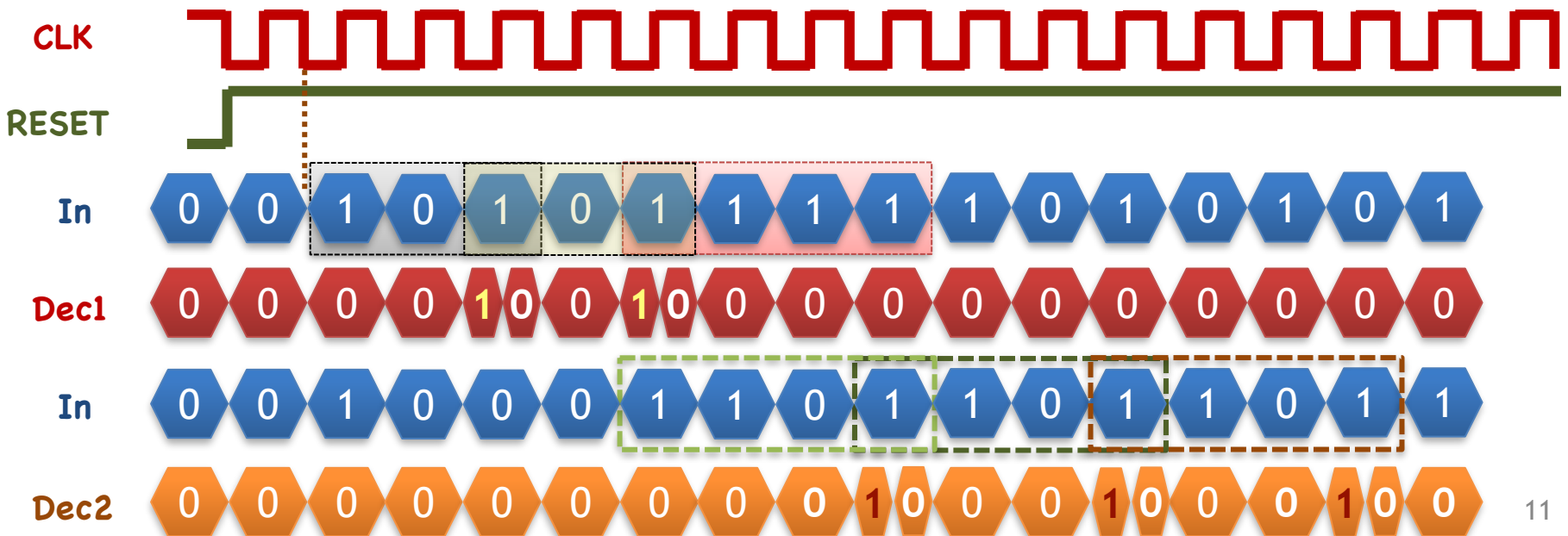
# Verilog Question 1

- Sliding Window sequence detector (**mealy machine**)
  - Dec1 == 1'b1 when input is **101** AND no **1111** occurs before
  - Dec2 == 1'b1 when input sequence is **1101**
- Continuous detection
  - Detect the sequences whenever they occur
  - Please draw a state transition diagram in your report



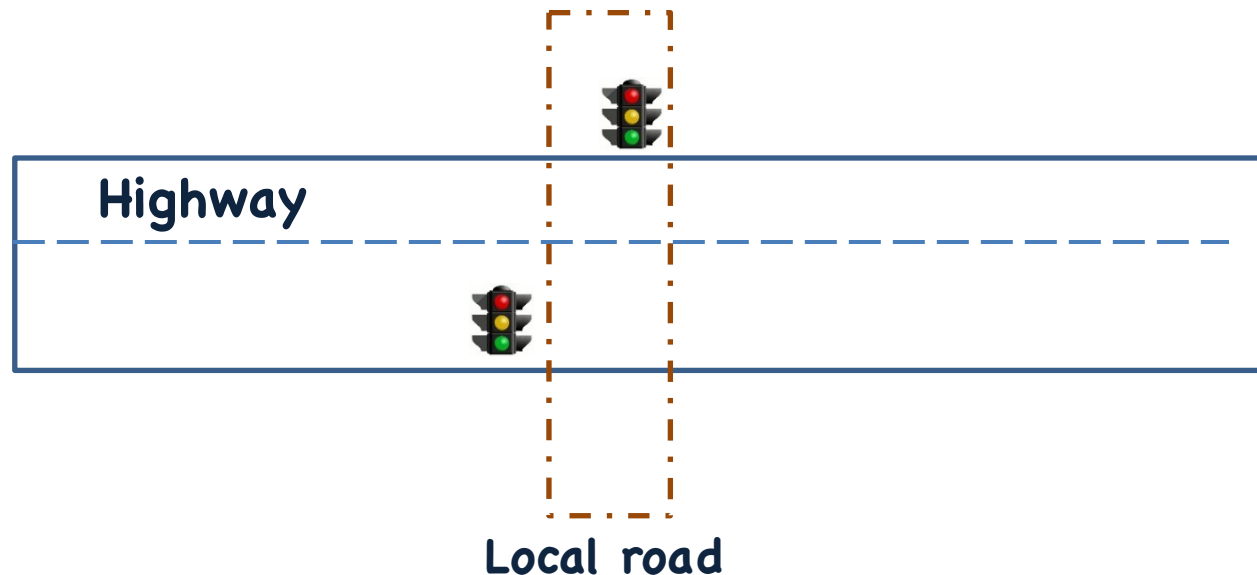
# Verilog Question 2

- **Traffic light controller** for highway (HW) and local road (LR) intersection
- **HW** has higher priority and should be green as long as possible
- **LR** has a sensor to detect cars on it. When a car is sensed, LR turns green shortly
- Green light is **at least 35** clock cycles and yellow light is **15** clock cycles
- **Input:** **CLK**, **RESET**, LR\_has\_Car; **Output:** HW\_light[2:0], LR\_light[2:0]
- HW\_light & LR\_light: bits [2:0] represent **Green**, **Yellow**, and **Red**, respectively



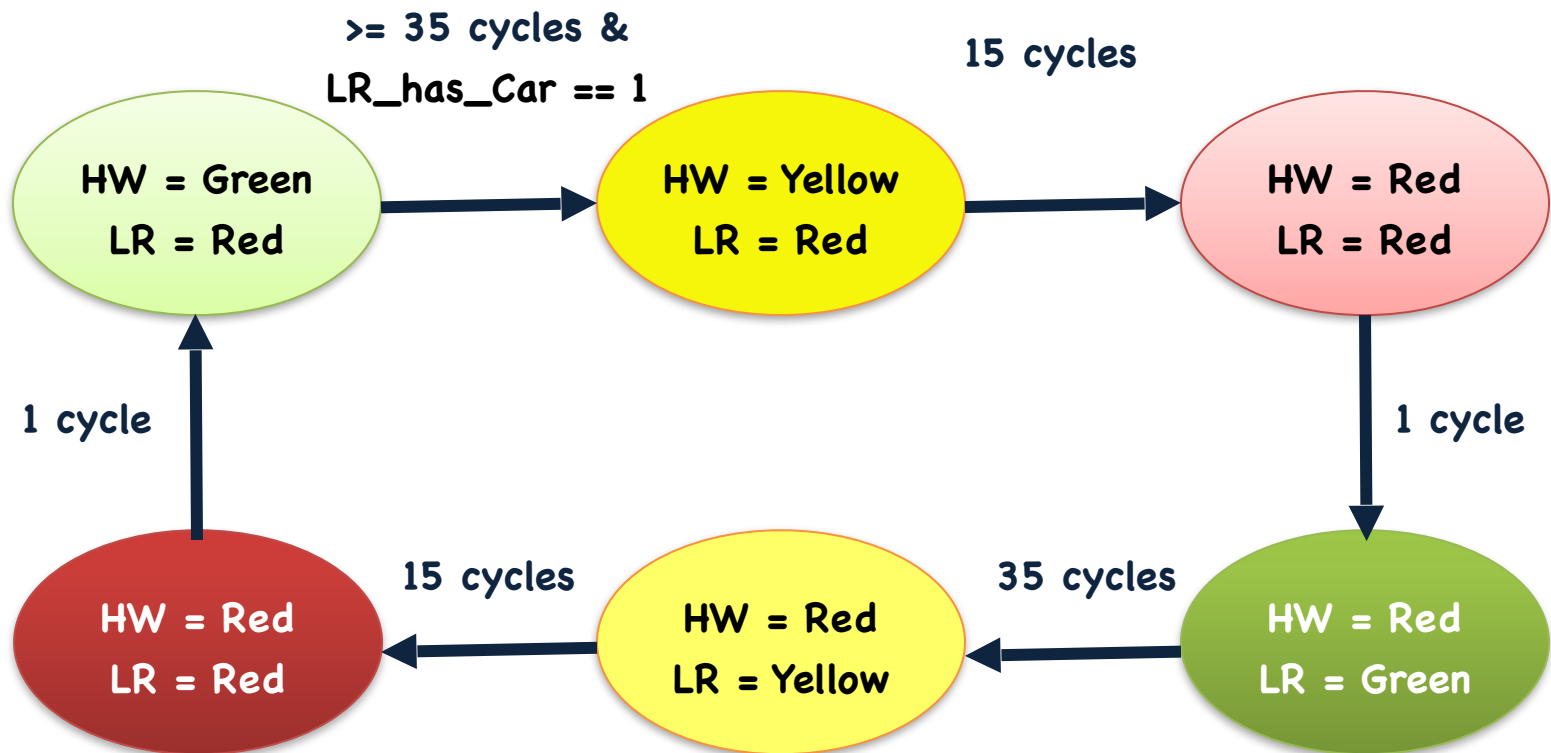
# Verilog Question 2

- Traffic light controller Finite State Machine
- Please complete the FSM in your report (some arrows are removed intentionally)



# Verilog Question 2

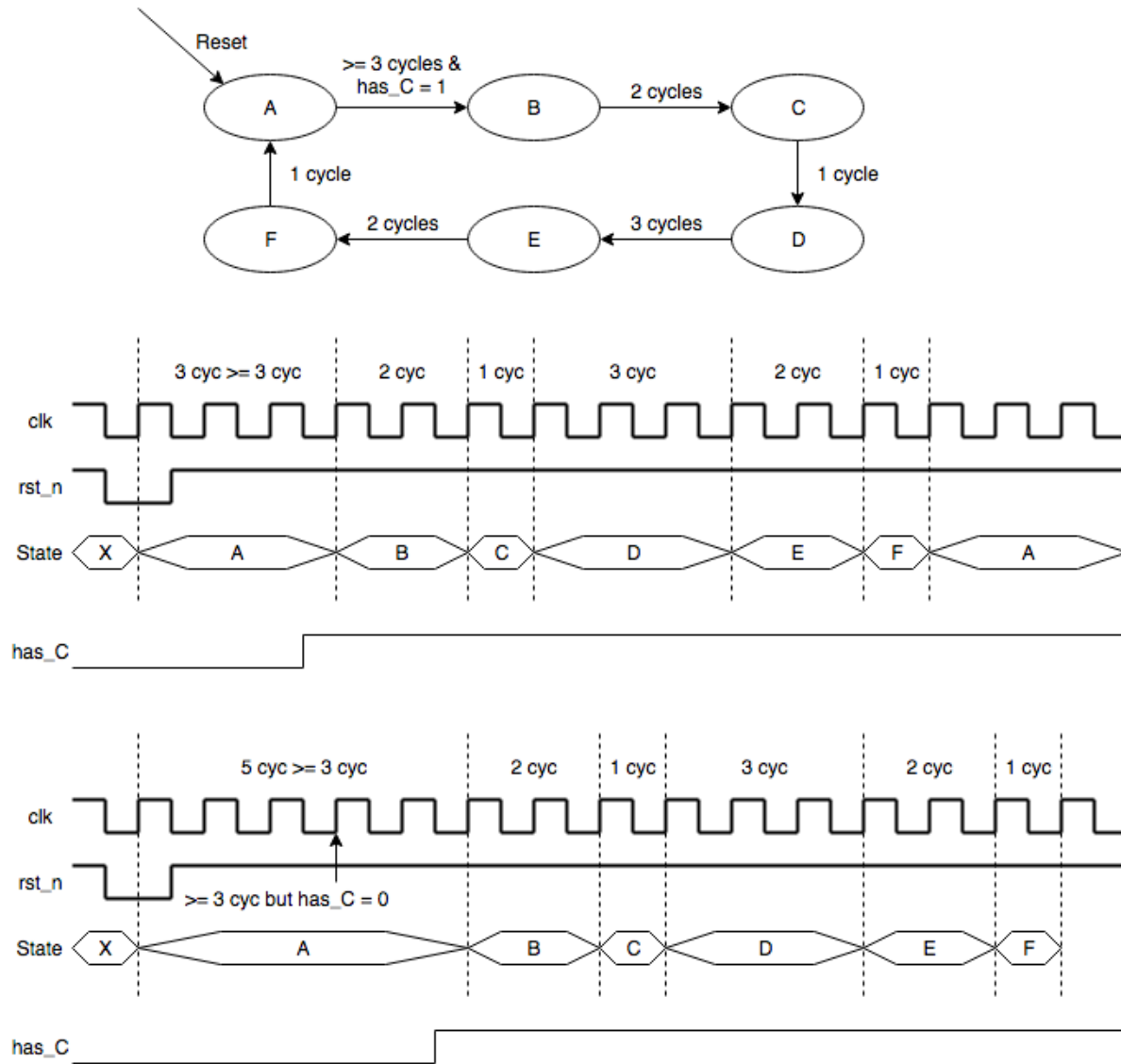



- Traffic light controller **"example"** timing diagram is illustrated on the left
- Please make sure that your state transitions follows the timing diagram correctly

# Advanced Questions

- Group assignment
- Verilog questions
  - Source codes and the report due on 11/26/2020. 23:59:59.
  - Sliding window sequence detector
  - Traffic light controller
- **FPGA demonstration** (due on 11/26/2020. In class.)
  - Mixed keyboard and audio modules together
  - Vending machine
  - Please submit your source codes by 11/26/2020. 15:00:00.
  - **We will only grade your demonstration based on your codes downloaded from ILMS.**

# FPGA Demonstration 1

- Use the numbers ("0" and "1") on the keyboard to control the scale to ascend or descend, ranging from **C4** to high **C8**.
- Change a note every **0.5 second**. If "2" is pressed, change a note every 1 second. If "2" is pressed again, go back to **0.5 second** per note.
- When it reaches **C4** or **C8**, stay on the note until the direction changes (keyboard pressed).

Button	Direction Reset: Set back to C4 and ascend (0.5sec/note) (Use Enter as Reset)
0	 <p>C4 D4 E4 F4 G4 A4 B4 C5 D5 E5 F5 G5 A5 B5 C6</p>
1	 <p>C4 D4 E4 F4 G4 A4 B4 C5 D5 E5 F5 G5 A5 B5 C6</p>
2	0.5 sec per note or 1 sec per note



# FPGA Demonstration 2

- Four options available: **Coffee**, **Coke**, **Oolong**, and **Water**
- Prices are: **Coffee** (NT\$ 60), **Coke** (NT\$ 30), **Oolong** (NT\$ 25), **Water** (NT\$ 20)
- The **rightmost two 7-segment displays** show the money inserted into the machine
  - When RESET == **1'b1**, please display "00"
  - The maximum value is **NT\$ 99**
- Use **five buttons** to implement your design:
  - Left: **NT\$ 5**
  - Center: **NT\$ 10**
  - Right: **NT\$ 50**
  - Top: **RESET**
  - Bottom: **Cancel**



# FPGA Demonstration 2

- Use **four LEDs** to indicate which drinks you can buy
  - **LED[3:0]** corresponds to Coffee, Coke, Oolong, and Water, respectively
- Use the **keyboard** to select which drinks you can buy
  - **'a', 's', 'd', 'f'** corresponds to **Coffee**, **Coke**, **Oolong**, and **Water**, respectively
  - Assume that the machine allows you to buy **ONLY ONE DRINK** at a time
- Use the **rightmost two 7-segment display** to **show the rest of the money** after buying a drink
  - E.g., if you inserted **NT\$ 40** and bought a can of **Oolong (NT\$ 25)**, the 7-segment display will show **NT\$ 15**

# FPGA Demonstration 2

- Remember to add debounce and one-pulse circuits to your buttons
- Decrement the **7-segment display** by **NT\$ 5** every second to mimic the process of returning changes
  - Return the changes until it becomes zero
- If the buyer does not want to buy a drink, he/she can use a **Cancel Button** to cancel it
  - The inserted money will be returned the same way (**NT\$ 5** per second)

The layout of the  
buttons used in this  
question



Insert  
NT\$ 5



RESET



Insert  
NT\$ 10



Insert  
NT\$ 50



Cancel



# Thank you for your attention!



\*Lake Helen at Lassen Volcanic National Park, Shasta County, California, USA  
This picture is taken by Chun-Yi Lee himself, who is also a fan of photography